

Group members

Group 34

Name: Rathnayaka W.T

Index: 210536K

Name: Dewpura L.C.I.K

Index:210116A

Lab 9-10

1)Assigned lab task

The task was to design a 4-bit processor capable of executing 4 instruction types. Other sub tasks of this lab was to design a 4-bit arithmetic unit that can add and subtract signed integers, decode instructions to activate necessary components on the processor, design k-way b-bit multiplexers or tri-state busses and finally test their functionality via simulation.

2) Assembly program and its machine code representation

Assembly Program

MOVI R7,0

MOVI R1,1

MOVI R2,2

MOVI R3,3

ADD R7,R1

ADD R7,R2

ADD R7,R3

JZR R0,6

Machine code

101110000000

100010000001

100100000010

100110000011

001110010000

001110100000

001110110000

110000000111

3) All VHDL Codes

4-bit adder subtractor unit

Sources

ASUnit.vhd

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity ASUnit is

Port (A : in STD_LOGIC_VECTOR (3 downto 0);

B : in STD_LOGIC_VECTOR (3 downto 0);

Selector : in STD_LOGIC;

S : out STD_LOGIC_VECTOR (3 downto 0);

Zero : out STD_LOGIC;

Overflow : out STD_LOGIC);

end ASUnit;

architecture Behavioral of ASUnit is

component FA

Port(A : in STD_LOGIC ;

B : in STD_LOGIC ;

C_in : in STD_LOGIC;

S : out STD_LOGIC;

C_out : out STD_LOGIC) ;

end component ;

signal FA0_C, FA1_C, FA2_C, FA3_C : STD_LOGIC ; -- Carry out of each Full Adder

signal FA0_B, FA1_B, FA2_B, FA3_B : STD_LOGIC ; -- B input of each Full Adder

signal FA0_S, FA1_S, FA2_S, FA3_S : STD_LOGIC ; -- S out of each Full Adder

begin

FA_0 : FA

port map (

```
A => A(0),
B => FA0_B,
C_in => Selector,
S => FA0_S,
C_Out => FA0_C);
```

```
FA_1 : FA
port map (
A => A(1),
B => FA1_B,
C_in => FA0_C,
S => FA1_S,
C_Out => FA1_C);
```

```
FA_2 : FA
port map (
A => A(2),
B => FA2_B,
C_in => FA1_C,
S => FA2_S,
C_Out => FA2_C);
```

```
FA_3 : FA
port map (
A => A(3),
B => FA3_B,
C_in => FA2_C,
S => FA3_S,
C_Out => FA3_C);
```

```
-- define B input for each FA
```

```
FA0_B <= Selector XOR B(0) ;
FA1_B <= Selector XOR B(1) ;
FA2_B <= Selector XOR B(2) ;
FA3_B <= Selector XOR B(3) ;
```

```
-- Overflow = C3 XOR C4
```

```
Overflow <= FA2_C XOR FA3_C ;
```

```
-- If 0000 then Zero = 1
```

```
Zero <= (NOT(FA0_S)) AND (NOT(FA1_S)) AND (NOT(FA2_S)) AND (NOT(FA3_S)) ;
```

```
-- Define S outputs
```

```
S(0) <= FA0_S ;
```

```
S(1) <= FA1_S ;
```

```
S(2) <= FA2_S ;
```

```
S(3) <= FA3_S ;
```

```
end Behavioral;
```

FA.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity FA is
```

```
    Port ( A : in STD_LOGIC;
```

```
          B : in STD_LOGIC;
```

```
          C_in : in STD_LOGIC;
```

```
          S : out STD_LOGIC;
```

```
          C_out : out STD_LOGIC);
```

```
end FA;
```

```
architecture Behavioral of FA is
```

```
    component HA
```

```
    port (
```

```
        A: in std_logic;
```

```
        B: in std_logic;
```

```
        S: out std_logic;
```

```
        C: out std_logic);
```

```
end component;
```

```
SIGNAL HA0_S, HA0_C, HA1_S, HA1_C : std_logic;
```

```
begin
```

```
    HA_0 : HA
```

```
    port map (
```

```
        A => A,
```

```
        B => B,
```

```
        S => HA0_S,
```

```
C => HA0_C);
```

```
HA_1 : HA  
port map (  
A => HA0_S,  
B => C_in,  
S => HA1_S,  
C => HA1_C);
```

```
S <= HA1_S;  
C_out <= HA0_C OR HA1_C;
```

```
end Behavioral;
```

HA.vhd

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity HA is  
  Port ( A : in STD_LOGIC;  
        B : in STD_LOGIC;  
        S : out STD_LOGIC;  
        C : out STD_LOGIC);  
end HA;
```

```
architecture Behavioral of HA is
```

```
begin  
  S <= A XOR B;  
  C <= A AND B;
```

```
end Behavioral;
```

Simulations

TB_ASUnit.vhd

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

entity TB_ASUnit is

-- Port ();

end TB_ASUnit;

architecture Behavioral of TB_ASUnit is

component ASUnit

Port (A : in STD_LOGIC_VECTOR (3 downto 0);

B : in STD_LOGIC_VECTOR (3 downto 0);

Selector : in STD_LOGIC;

S : out STD_LOGIC_VECTOR (3 downto 0);

Zero : out STD_LOGIC;

Overflow : out STD_LOGIC);

end component;

signal A : STD_LOGIC_VECTOR (3 downto 0);

signal B : STD_LOGIC_VECTOR (3 downto 0);

signal Selector : STD_LOGIC;

signal S : STD_LOGIC_VECTOR (3 downto 0);

signal Zero : STD_LOGIC;

signal Overflow : STD_LOGIC;

begin

UUT : ASUnit PORT MAP (

A => A,

B => B,

Selector => Selector,

S => S,

Zero => Zero,

Overflow => Overflow

);

--Index 210536 - 11 0011 0110 0110 1000

--Index 210116 - 11 0011 0100 1100 0100

process

begin

-- $1000 + 0110 = 1110$

A <= "1000";

B <= "0110";

Selector <= '0'; -- add

WAIT FOR 100ns ;

-- $1100 + 0110 = 1\ 0010$

A <= "1100";

B <= "0110";

Selector <= '0'; -- add

WAIT FOR 100ns ;

-- $1100 - 0110 = 0110$

A <= "1100";

B <= "0110";

Selector <= '1'; -- sub

WAIT FOR 100ns ;

-- $0011 - 0100 = 1111$

A <= "0011";

B <= "0100";

Selector <= '1'; -- sub

WAIT FOR 100ns ;

-- $0011 - 0011 = 0000$ -- check Zero flag

A <= "0011";

B <= "0011";

Selector <= '1'; -- add

WAIT ;

end process;

end Behavioral;

3-bit adder

Sources

Adder_3bit.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Adder_3bit is
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
          S : out STD_LOGIC_VECTOR (2 downto 0));
end Adder_3bit;

architecture Behavioral of Adder_3bit is

    component FA
        Port( A : in STD_LOGIC ;
              B : in STD_LOGIC ;
              C_in : in STD_LOGIC;
              S : out STD_LOGIC;
              C_out : out STD_LOGIC );
    end component ;

    signal FA0_C, FA1_C, FA2_C : STD_LOGIC ; -- Carry out of each Full Adder
    signal B : STD_LOGIC_VECTOR (2 downto 0) ; -- B input 001 always as a 3 bit bus

begin

    B <= "001";

    FA_0 : FA
    port map (
        A => A(0),
        B => B(0),
        C_in => '0', -- No carry initially
```



```
S => S(0),  
C_Out => FA0_C);
```

```
FA_1 : FA  
port map (  
A => A(1),  
B => B(1) ,  
C_in => FA0_C,  
S => S(1) ,  
C_Out => FA1_C);
```

```
FA_2 : FA  
port map (  
A => A(2),  
B => B(2),  
C_in => FA1_C,  
S => S(2),  
C_Out => FA2_C);  
end Behavioral;
```

Simulations

TB_Adder_3bit.vhd

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity TB_Adder_3bit is  
-- Port ( );  
end TB_Adder_3bit;
```

architecture Behavioral of TB_Adder_3bit is

```
component Adder_3bit  
Port ( A : in STD_LOGIC_VECTOR (2 downto 0);  
S : out STD_LOGIC_VECTOR (2 downto 0));
```

```
end component;
```

```
signal A : STD_LOGIC_VECTOR (2 downto 0);  
signal S : STD_LOGIC_VECTOR (2 downto 0);
```

```
begin
```

```
UUT : Adder_3bit PORT MAP (  
    A => A,  
    S => S  
);
```

```
--Index 210536 - 110 011 011 001 101 000  
--Index 210116 - 110 011 010 011 000 100
```

```
process
```

```
begin
```

```
--output should be 001  
A <= "000";
```

```
WAIT FOR 100ns;
```

```
--output should be 010  
A <= "001";
```

```
WAIT FOR 100ns;
```

```
--output should be 011  
A <= "010";
```

```
WAIT FOR 100ns;
```

```
--output should be 100  
A <= "011";
```

```
WAIT FOR 100ns;
```

```
--output should be 101  
A <= "100";
```

```
WAIT FOR 100ns;
```

```
--output should be 110
```

```
A <= "101";
```

```
WAIT FOR 100ns;
```

```
--output should be 111
```

```
A <= "110";
```

```
WAIT;
```

```
end process;
```

```
end Behavioral;
```

3-bit Program Counter

Sources

ProgramCounter.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity ProgramCounter is
```

```
Port ( D : in STD_LOGIC_VECTOR (2 downto 0);
```

```
      Res : in STD_LOGIC;
```

```
      Clk : in STD_LOGIC;
```

```
      Q : out STD_LOGIC_VECTOR (2 downto 0));
```

```
end ProgramCounter;
```

```
architecture Behavioral of ProgramCounter is
```

```
begin
```

```
    process (Clk) begin
```

```

    if(rising_edge(Clk)) then
        if Res='1' then
            Q<="000";

        else
            Q<=D;

        end if;
    end if;
end process;

end Behavioral;

```

Simulations

TB_ProgramCounter.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_ProgramCounter is
    -- Port ( );
end TB_ProgramCounter;

architecture Behavioral of TB_ProgramCounter is

    component ProgramCounter

        Port ( D : in STD_LOGIC_VECTOR (2 downto 0);
              Res : in STD_LOGIC;
              Clk : in STD_LOGIC;
              Q : out STD_LOGIC_VECTOR (2 downto 0));

    end component;

    signal D : STD_LOGIC_VECTOR (2 downto 0);
    signal Res : STD_LOGIC;
    signal Clk : STD_LOGIC;
    signal Q : STD_LOGIC_VECTOR(2 downto 0);

```

```
constant period : time := 80 ns;
```

```
begin
```

```
UUT : ProgramCounter PORT MAP (
```

```
    D => D,
```

```
    Res=>Res,
```

```
    Clk=> Clk,
```

```
    Q => Q
```

```
);
```

```
process
```

```
begin
```

```
    Clk <= '0';
```

```
    wait for period/2;
```

```
    Clk <= '1';
```

```
    wait for period/2 ;
```

```
end process;
```

```
--Index 210536 - 110 011 011 001 101 000
```

```
--Index 210116 - 110 011 010 011 000 100
```

```
process
```

```
begin
```

```
Res <= '0';
```

```
D <= "000";
```

```
wait for period;
```

```
D <= "100";
```

```
wait for period;
```

```
D <= "011";
```

wait for period;

D <= "111";

wait for period;

Res <= '1';

wait for period;

Res <= '0';

D <= "101";

wait;

end process;

k-way b-bit multiplexers

Sources

Mux_2_to_1_bit_3.vhd (2-way 3-bit multiplexer)

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Mux_2_to_1_bit_3 is

Port (S : in STD_LOGIC;

D0 : in STD_LOGIC_VECTOR (2 downto 0);

D1 : in STD_LOGIC_VECTOR (2 downto 0);

Y : out STD_LOGIC_VECTOR (2 downto 0));

end Mux_2_to_1_bit_3;

architecture Behavioral of Mux_2_to_1_bit_3 is

component Mux_2_to_1

Port (S : in STD_LOGIC ;

```

        D : in STD_LOGIC_VECTOR (1 downto 0);
        EN : in STD_LOGIC;
        Y : out STD_LOGIC);
end component;

signal Mux_0_D,Mux_1_D,Mux_2_D : STD_LOGIC_VECTOR (1 downto 0);

begin

Mux_2_to_1_0 : Mux_2_to_1
port map(
    S => S ,
    D => Mux_0_D,
    EN=> '1',
    Y => Y(0)

);

Mux_2_to_1_1 : Mux_2_to_1
port map(
    S => S,
    D => Mux_1_D,
    EN=> '1',
    Y => Y(1)

);

Mux_2_to_1_2 : Mux_2_to_1
port map(
    S => S,
    D => Mux_2_D,
    EN=> '1',
    Y => Y(2)

);

-- inputs for mu;tiplexer 0

```

```

Mux_0_D(0) <= D0(0);
Mux_0_D(1) <= D1(0);

-- inputs for mu;tiplexer 1
Mux_1_D(0) <= D0(1);
Mux_1_D(1) <= D1(1);

-- inputs for mu;tiplexer 2
Mux_2_D(0) <= D0(2);
Mux_2_D(1) <= D1(2);

```

```

end Behavioral;

```

Mux_2_to_1.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux_2_to_1 is
    Port ( S : in STD_LOGIC;
          D : in STD_LOGIC_VECTOR (1 downto 0);
          EN : in STD_LOGIC;
          Y : out STD_LOGIC);
end Mux_2_to_1;

architecture Behavioral of Mux_2_to_1 is

    --If S = '0' then
    --    Y <= D(0)
    -- else
    --    Y <= D(1)

begin
Y <= ( (NOT(S) AND D(0) ) OR ( S AND D(1) ) ) AND EN ;

end Behavioral;

```


Mux_2_to_1_bit_4.vhd (2-way 4-bit multiplexer)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux_2_to_1_bit_4 is
    Port ( S : in STD_LOGIC;
          D0 : in STD_LOGIC_VECTOR (3 downto 0);
          D1 : in STD_LOGIC_VECTOR (3 downto 0);
          Y : out STD_LOGIC_VECTOR (3 downto 0));
end Mux_2_to_1_bit_4;

architecture Behavioral of Mux_2_to_1_bit_4 is

    component Mux_2_to_1
        Port ( S : in STD_LOGIC ;
              D : in STD_LOGIC_VECTOR (1 downto 0);
              EN : in STD_LOGIC;
              Y : out STD_LOGIC);
    end component;

    signal Mux_0_D,Mux_1_D,Mux_2_D,Mux_3_D : STD_LOGIC_VECTOR (1 downto 0);

begin

    Mux_2_to_1_0 : Mux_2_to_1
    port map(
        S => S ,
        D => Mux_0_D,
        EN=> '1',
        Y => Y(0)
    );

    Mux_2_to_1_1 : Mux_2_to_1
    port map(
        S => S,
        D => Mux_1_D,
```

```
EN=> '1',  
Y => Y(1)
```

```
);
```

```
Mux_2_to_1_2 : Mux_2_to_1  
port map(  
    S => S,  
    D => Mux_2_D,  
    EN=> '1',  
    Y => Y(2)
```

```
);
```

```
Mux_2_to_1_3 : Mux_2_to_1  
port map(  
    S => S,  
    D => Mux_3_D,  
    EN=> '1',  
    Y => Y(3)
```

```
);
```

```
-- inputs for mu;tiplexer 0  
Mux_0_D(0) <= D0(0);  
Mux_0_D(1) <= D1(0);
```

```
-- inputs for mu;tiplexer 1  
Mux_1_D(0) <= D0(1);  
Mux_1_D(1) <= D1(1);
```

```
-- inputs for mu;tiplexer 2  
Mux_2_D(0) <= D0(2);  
Mux_2_D(1) <= D1(2);
```

```
-- inputs for mu;tiplexer 3  
Mux_3_D(0) <= D0(3);
```

```
Mux_3_D(1) <= D1(3);
```

```
end Behavioral;
```

Mux_8_to_1_bit_4.vhd (8-way 4-bit multiplexer)

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Mux_8_to_1_bit_4 is
```

```
    Port ( S : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          D0 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          D1 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          D2 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          D3 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          D4 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          D5 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          D6 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          D7 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          Y : out STD_LOGIC_VECTOR (3 downto 0));
```

```
end Mux_8_to_1_bit_4;
```

```
architecture Behavioral of Mux_8_to_1_bit_4 is
```

```
    component Mux_8_to_1
```

```
        Port ( S : in STD_LOGIC_VECTOR (2 downto 0);
```

```
              D : in STD_LOGIC_VECTOR (7 downto 0);
```

```
              EN : in STD_LOGIC;
```

```
              Y : out STD_LOGIC);
```

```
    end component;
```

```
    signal Mux_0_D,Mux_1_D,Mux_2_D,Mux_3_D : STD_LOGIC_VECTOR (7 downto 0);
```

```
begin
```

```
    Mux_8_to_1_0 : Mux_8_to_1
```

```
    port map(
```

```

    S => S,
    D => Mux_0_D,
    EN=> '1',
    Y => Y(0)

);

Mux_8_to_1_1 : Mux_8_to_1
port map(
    S => S,
    D => Mux_1_D,
    EN=> '1',
    Y => Y(1)

);

Mux_8_to_1_2 : Mux_8_to_1
port map(
    S => S,
    D => Mux_2_D,
    EN=> '1',
    Y => Y(2)
);

Mux_8_to_1_3 : Mux_8_to_1
port map(
    S => S,
    D => Mux_3_D,
    EN=> '1',
    Y => Y(3)
);

-- inputs for multiplexer 0
Mux_0_D(0) <= D0(0);
Mux_0_D(1) <= D1(0);
Mux_0_D(2) <= D2(0);
Mux_0_D(3) <= D3(0);
Mux_0_D(4) <= D4(0);
Mux_0_D(5) <= D5(0);
Mux_0_D(6) <= D6(0);

```

```

Mux_0_D(7) <= D7(0);

-- inputs for mu;tiplexer 1
Mux_1_D(0) <= D0(1);
Mux_1_D(1) <= D1(1);
Mux_1_D(2) <= D2(1);
Mux_1_D(3) <= D3(1);
Mux_1_D(4) <= D4(1);
Mux_1_D(5) <= D5(1);
Mux_1_D(6) <= D6(1);
Mux_1_D(7) <= D7(1);

-- inputs for mu;tiplexer 2
Mux_2_D(0) <= D0(2);
Mux_2_D(1) <= D1(2);
Mux_2_D(2) <= D2(2);
Mux_2_D(3) <= D3(2);
Mux_2_D(4) <= D4(2);
Mux_2_D(5) <= D5(2);
Mux_2_D(6) <= D6(2);
Mux_2_D(7) <= D7(2);

-- inputs for mu;tiplexer 3
Mux_3_D(0) <= D0(3);
Mux_3_D(1) <= D1(3);
Mux_3_D(2) <= D2(3);
Mux_3_D(3) <= D3(3);
Mux_3_D(4) <= D4(3);
Mux_3_D(5) <= D5(3);
Mux_3_D(6) <= D6(3);
Mux_3_D(7) <= D7(3);

end Behavioral;

```

Mux_8_to_1.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity Mux_8_to_1 is
  Port ( S : in STD_LOGIC_VECTOR (2 downto 0);
        D : in STD_LOGIC_VECTOR (7 downto 0);
        EN : in STD_LOGIC;
        Y : out STD_LOGIC);
end Mux_8_to_1;

```

architecture Behavioral of Mux_8_to_1 is

```

component Decoder_3_to_8
port(
I: in STD_LOGIC_VECTOR;
EN: in STD_LOGIC;
Y: out STD_LOGIC_VECTOR );
end component;

```

```

signal S0 : STD_LOGIC_VECTOR (2 downto 0);
signal Y0 : STD_LOGIC_VECTOR (7 downto 0);
signal
en0,minTerm_0,minTerm_1,minTerm_2,minTerm_3,minTerm_4,minTerm_5,minTerm_6,minTerm_7 : STD_LOGIC;

```

```

begin
Decoder_3_to_8_0 : Decoder_3_to_8
port map(
I => S0,
EN => en0,
Y => Y0 );

```

```

en0 <= EN;
S0 <= S;

```

```

minTerm_0 <= Y0(0) AND D(0);
minTerm_1 <= Y0(1) AND D(1);
minTerm_2 <= Y0(2) AND D(2);
minTerm_3 <= Y0(3) AND D(3);
minTerm_4 <= Y0(4) AND D(4);
minTerm_5 <= Y0(5) AND D(5);
minTerm_6 <= Y0(6) AND D(6);
minTerm_7 <= Y0(7) AND D(7);

```

```
Y <= minTerm_0 OR minTerm_1 OR minTerm_2 OR minTerm_3 OR minTerm_4 OR  
minTerm_5 OR minTerm_6 OR minTerm_7;
```

```
end Behavioral;
```

Decoder_3_to_8.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Decoder_3_to_8 is
```

```
    Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          EN : in STD_LOGIC;
```

```
          Y : out STD_LOGIC_VECTOR (7 downto 0));
```

```
end Decoder_3_to_8;
```

```
architecture Behavioral of Decoder_3_to_8 is
```

```
    component Decoder_2_to_4
```

```
    port(
```

```
        I: in STD_LOGIC_VECTOR;
```

```
        EN: in STD_LOGIC;
```

```
        Y: out STD_LOGIC_VECTOR );
```

```
    end component;
```

```
    signal I0,I1 : STD_LOGIC_VECTOR (1 downto 0);
```

```
    signal Y0,Y1 : STD_LOGIC_VECTOR (3 downto 0);
```

```
    signal en0,en1, I2 : STD_LOGIC;
```

```
begin
```

```
    Decoder_2_to_4_0 : Decoder_2_to_4
```

```
    port map(
```

```
        I => I0,
```

```
        EN => en0,
```

```
        Y => Y0 );
```

```
    Decoder_2_to_4_1 : Decoder_2_to_4
```

```
    port map(
```

```

I => I1,
EN => en1,
Y => Y1 );
en0 <= NOT(I(2)) AND EN;
en1 <= I(2) AND EN;
I0 <= I(1 downto 0);
I1 <= I(1 downto 0);
I2 <= I(2);
Y(3 downto 0) <= Y0;
Y(7 downto 4) <= Y1;

end Behavioral;

```

Decoder_2_to_4.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Decoder_2_to_4 is
    Port ( I : in STD_LOGIC_VECTOR (1 downto 0);
          EN : in STD_LOGIC;
          Y : out STD_LOGIC_VECTOR (3 downto 0));
end Decoder_2_to_4;

architecture Behavioral of Decoder_2_to_4 is

begin

Y(0) <= NOT(I(0)) AND NOT(I(1)) AND EN;
Y(1) <= I(0) AND NOT(I(1)) AND EN;
Y(2) <= NOT(I(0)) AND I(1) AND EN;
Y(3) <= I(0) AND I(1) AND EN;

end Behavioral;

```

Simulations

TB_Mux_2_to_1_bit_3.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Mux_2_to_1_bit_3 is
-- Port ( );
end TB_Mux_2_to_1_bit_3;

architecture Behavioral of TB_Mux_2_to_1_bit_3 is

component Mux_2_to_1_bit_3
    Port( S : in STD_LOGIC;
          D0 : in STD_LOGIC_VECTOR (2 downto 0);
          D1 : in STD_LOGIC_VECTOR (2 downto 0);
          Y : out STD_LOGIC_VECTOR (2 downto 0));
end component;

signal S : STD_LOGIC;
signal D0: STD_LOGIC_VECTOR(2 downto 0);
signal D1: STD_LOGIC_VECTOR(2 downto 0);
signal Y : STD_LOGIC_VECTOR(2 downto 0);

begin

UUT : Mux_2_to_1_bit_3 PORT MAP (
    S => S ,
    D0 => D0,
    D1 => D1,
    Y => Y
);

--Index 210536 - 110 011 011 001 101 000
--Index 210116 - 110 011 010 011 000 100

process

begin

--output should be "011"
```

```

S <= '1' ;
D0 <= "110";
D1 <= "011";

WAIT FOR 100 ns;

--output should be "011"
S <= '0';
D0 <= "011";
D1 <= "001";

WAIT FOR 100 ns;

--output should be "000"
S <= '1';
D0 <= "101";
D1 <= "000";

WAIT FOR 100 ns;

--output should be "010"
S <= '0';
D0 <= "010";
D1 <= "011";

WAIT;

end process;

end Behavioral;

```

TB_Mux_2_to_1_bit_4.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Mux_2_to_1_bit_4 is
-- Port ( );
end TB_Mux_2_to_1_bit_4;

```

architecture Behavioral of TB_Mux_2_to_1_bit_4 is

component Mux_2_to_1_bit_4

Port(S : in STD_LOGIC;

D0 : in STD_LOGIC_VECTOR (3 downto 0);

D1 : in STD_LOGIC_VECTOR (3 downto 0);

Y : out STD_LOGIC_VECTOR (3 downto 0));

end component;

signal S : STD_LOGIC;

signal D0: STD_LOGIC_VECTOR(3 downto 0);

signal D1: STD_LOGIC_VECTOR(3 downto 0);

signal Y : STD_LOGIC_VECTOR(3 downto 0);

begin

UUT : Mux_2_to_1_bit_4 PORT MAP (

S => S ,

D0 => D0,

D1 => D1,

Y => Y

);

--Index 210536 - 11 0011 0110 0110 1000

--Index 210116 - 11 0011 0100 1100 0100

process

begin

--output should be "0110"

S <= '1' ;

D0 <= "1000";

D1 <= "0110";

WAIT FOR 100 ns;

--output should be "0011"

S <= '0';

```
D0 <= "0011";  
D1 <= "0110";
```

```
WAIT FOR 100 ns;
```

```
--output should be "1100"  
S <= '1';  
D0 <= "0100";  
D1 <= "1100";
```

```
WAIT FOR 100 ns;
```

```
--output should be "1000"  
S <= '0';  
D0 <= "1000";  
D1 <= "0100";
```

```
WAIT;
```

```
end process;
```

```
end Behavioral;
```

TB_Mux_8_to_1_bit_4.vhd

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity TB_Mux_8_to_1_bit_4 is  
-- Port ( );  
end TB_Mux_8_to_1_bit_4;
```

```
architecture Behavioral of TB_Mux_8_to_1_bit_4 is
```

```
component Mux_8_to_1_bit_4  
Port ( S : in STD_LOGIC_VECTOR (2 downto 0);  
      D0 : in STD_LOGIC_VECTOR (3 downto 0);  
      D1 : in STD_LOGIC_VECTOR (3 downto 0);  
      D2 : in STD_LOGIC_VECTOR (3 downto 0);  
      D3 : in STD_LOGIC_VECTOR (3 downto 0);
```

```

        D4 : in STD_LOGIC_VECTOR (3 downto 0);
        D5 : in STD_LOGIC_VECTOR (3 downto 0);
        D6 : in STD_LOGIC_VECTOR (3 downto 0);
        D7 : in STD_LOGIC_VECTOR (3 downto 0);
        Y : out STD_LOGIC_VECTOR (3 downto 0));
end component;

```

```

signal S : STD_LOGIC_VECTOR (2 downto 0);
signal D0 : STD_LOGIC_VECTOR (3 downto 0);
signal D1 : STD_LOGIC_VECTOR (3 downto 0);
signal D2 : STD_LOGIC_VECTOR (3 downto 0);
signal D3 : STD_LOGIC_VECTOR (3 downto 0);
signal D4 : STD_LOGIC_VECTOR (3 downto 0);
signal D5 : STD_LOGIC_VECTOR (3 downto 0);
signal D6 : STD_LOGIC_VECTOR (3 downto 0);
signal D7 : STD_LOGIC_VECTOR (3 downto 0);
signal Y : STD_LOGIC_VECTOR (3 downto 0);

```

```
begin
```

```

UUT : Mux_8_to_1_bit_4 PORT MAP(
    S=>S,
    D0=>D0,
    D1=>D1,
    D2=>D2,
    D3=>D3,
    D4=>D4,
    D5=>D5,
    D6=>D6,
    D7=>D7,
    Y=>Y
);

```

```

--Index 210536 - 11 0011 0110 0110 1000
--Index 210116 - 11 0011 0100 1100 0100

```

```

process
begin

```

```
--select D0
```

```
S <= "000";  
D0<= "0011";  
D0<= "0110";  
D1<= "1110";  
D2<= "1000";  
D3<= "1011";  
D4<= "0100";  
D5<= "1100";  
D6<= "0101";  
D7<= "0000";
```

```
wait for 100 ns;
```

```
--select D1  
S <= "001";  
D0<= "0011";  
D0<= "0110";  
D1<= "1110";  
D2<= "1000";  
D3<= "1011";  
D4<= "0100";  
D5<= "1100";  
D6<= "0101";  
D7<= "0000";
```

```
wait for 100 ns;
```

```
--select D2  
S <= "010";  
D0<= "0011";  
D0<= "0110";  
D1<= "1110";  
D2<= "1000";  
D3<= "1011";  
D4<= "0100";  
D5<= "1100";  
D6<= "0101";  
D7<= "0000";
```

```
wait for 100 ns;
```

```
--select D3
S <= "011";
D0<= "0011";
D0<= "0110";
D1<= "1110";
D2<= "1000";
D3<= "1011";
D4<= "0100";
D5<= "1100";
D6<= "0101";
D7<= "0000";
```

```
wait for 100 ns;
```

```
--select D4
S <= "100";
D0<= "0011";
D0<= "0110";
D1<= "1110";
D2<= "1000";
D3<= "1011";
D4<= "0100";
D5<= "1100";
D6<= "0101";
D7<= "0000";
```

```
wait for 100 ns;
```

```
--select D5
S <= "101";
D0<= "0011";
D0<= "0110";
D1<= "1110";
D2<= "1000";
D3<= "1011";
D4<= "0100";
D5<= "1100";
D6<= "0101";
```

```
D7<= "0000";
```

```
wait for 100 ns;
```

```
--select D6
```

```
S <= "110";
```

```
D0<= "0011";
```

```
D0<= "0110";
```

```
D1<= "1110";
```

```
D2<= "1000";
```

```
D3<= "1011";
```

```
D4<= "0100";
```

```
D5<= "1100";
```

```
D6<= "0101";
```

```
D7<= "0000";
```

```
wait for 100 ns;
```

```
--select D7
```

```
S <= "111";
```

```
D0<= "0011";
```

```
D0<= "0110";
```

```
D1<= "1110";
```

```
D2<= "1000";
```

```
D3<= "1011";
```

```
D4<= "0100";
```

```
D5<= "1100";
```

```
D6<= "0101";
```

```
D7<= "0000";
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```


Register Bank

Sources

RegBank.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RegBank is
    Port (
        RegBank_EN : in STD_LOGIC_VECTOR(2 downto 0); -- Register enable which selects the
register
        RegBank_Clk : in STD_LOGIC;
        RegBank_Res : in STD_LOGIC ;
        RegBank_D : in STD_LOGIC_VECTOR(3 downto 0); -- input of register bank

        -- output of register bank
        RegBank_Q_0 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 0
        RegBank_Q_1 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 1
        RegBank_Q_2 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 2
        RegBank_Q_3 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 3
        RegBank_Q_4 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 4
        RegBank_Q_5 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 5
        RegBank_Q_6 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 6
        RegBank_Q_7 : out STD_LOGIC_VECTOR(3 downto 0) -- output of register 7
    );
end RegBank;

architecture Behavioral of RegBank is

    component Reg_4_bit
        Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
            EN : in STD_LOGIC;
            Res : in STD_LOGIC;
            Clk : in STD_LOGIC;
            Q : out STD_LOGIC_VECTOR (3 downto 0));
    end component;
```

```

component Decoder_3_to_8
  Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
        EN : in STD_LOGIC;
        Y : out STD_LOGIC_VECTOR (7 downto 0));
end component ;

signal Decoder_output : STD_LOGIC_VECTOR(7 downto 0);
signal RegBank_Q_0_temp : STD_LOGIC_VECTOR(3 downto 0);

begin

RegBank_Decoder_3_to_8 : Decoder_3_to_8
port map(
  I => RegBank_EN ,
  EN=> '1',
  Y => Decoder_output
);

Reg_4_bit_0 : Reg_4_bit
port map(
  D => "0000", --hardcode Register 0 into "0000"
  EN=> Decoder_output(0),
  Res=>RegBank_Res,
  Clk=>RegBank_Clk,
  Q=>RegBank_Q_0_temp
);

Reg_4_bit_1 : Reg_4_bit
port map(
  D => RegBank_D,
  EN=> Decoder_output(1),
  Res=>RegBank_Res,
  Clk=>RegBank_Clk,
  Q=>RegBank_Q_1
);

Reg_4_bit_2 : Reg_4_bit
port map(

```

```
D => RegBank_D,  
EN=> Decoder_output(2),  
Res=>RegBank_Res,  
Clk=>RegBank_Clk,  
Q=>RegBank_Q_2  
);
```

```
Reg_4_bit_3 : Reg_4_bit  
port map(  
  D => RegBank_D,  
  EN=> Decoder_output(3),  
  Res=>RegBank_Res,  
  Clk=>RegBank_Clk,  
  Q=>RegBank_Q_3  
);
```

```
Reg_4_bit_4 : Reg_4_bit  
port map(  
  D => RegBank_D,  
  EN=> Decoder_output(4),  
  Res=>RegBank_Res,  
  Clk=>RegBank_Clk,  
  Q=>RegBank_Q_4  
);
```

```
Reg_4_bit_5 : Reg_4_bit  
port map(  
  D => RegBank_D,  
  EN=> Decoder_output(5),  
  Res=>RegBank_Res,  
  Clk=>RegBank_Clk,  
  Q=>RegBank_Q_5  
);
```

```
Reg_4_bit_6 : Reg_4_bit  
port map(  
  D => RegBank_D,  
  EN=> Decoder_output(6),  
  Res=>RegBank_Res,  
  Clk=>RegBank_Clk,
```

```

        Q=>RegBank_Q_6
    );

    Reg_4_bit_7 : Reg_4_bit
    port map(
        D => RegBank_D,
        EN=> Decoder_output(7),
        Res=>RegBank_Res,
        Clk=>RegBank_Clk,
        Q=>RegBank_Q_7
    );
    RegBank_Q_0 <= "0000";
end Behavioral;

```

Reg_4_bit.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Reg_4_bit is
    Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
          EN : in STD_LOGIC;
          Res : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (3 downto 0));
end Reg_4_bit;

architecture Behavioral of Reg_4_bit is

begin

    process (Clk) begin
        if(rising_edge(Clk)) then
            if En = '1' then
                if Res='1' then
                    Q<="0000";

```

```

        else
            Q<=D;

        end if;
    end if;
end if;
end process;

end Behavioral;

```

Simulations

TB_RegBank.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_RegBank is
    -- Port ( );
end TB_RegBank;

architecture Behavioral of TB_RegBank is

    component RegBank

        Port (
            RegBank_EN : in STD_LOGIC_VECTOR(2 downto 0); -- Register enable which selects the
            register
            RegBank_Clk : in STD_LOGIC;
            RegBank_Res : in STD_LOGIC ;
            RegBank_D : in STD_LOGIC_VECTOR(3 downto 0); -- input of register bank

            -- output of register bank
            RegBank_Q_0 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 0
            RegBank_Q_1 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 1
            RegBank_Q_2 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 2
            RegBank_Q_3 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 3
            RegBank_Q_4 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 4

```

```
RegBank_Q_5 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 5
RegBank_Q_6 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 6
RegBank_Q_7 : out STD_LOGIC_VECTOR(3 downto 0) -- output of register 7
);
end component;
```

```
signal RegBank_EN : STD_LOGIC_VECTOR(2 downto 0); -- Register enable which selects the
register
```

```
signal RegBank_Clk : STD_LOGIC;
```

```
signal RegBank_Res : STD_LOGIC ;
```

```
signal RegBank_D : STD_LOGIC_VECTOR(3 downto 0); -- input of register bank
```

```
-- output of register bank
```

```
signal RegBank_Q_0 : STD_LOGIC_VECTOR(3 downto 0); -- output of register 0
```

```
signal RegBank_Q_1 : STD_LOGIC_VECTOR(3 downto 0); -- output of register 1
```

```
signal RegBank_Q_2 : STD_LOGIC_VECTOR(3 downto 0); -- output of register 2
```

```
signal RegBank_Q_3 : STD_LOGIC_VECTOR(3 downto 0); -- output of register 3
```

```
signal RegBank_Q_4 : STD_LOGIC_VECTOR(3 downto 0); -- output of register 4
```

```
signal RegBank_Q_5 : STD_LOGIC_VECTOR(3 downto 0); -- output of register 5
```

```
signal RegBank_Q_6 : STD_LOGIC_VECTOR(3 downto 0); -- output of register 6
```

```
signal RegBank_Q_7 : STD_LOGIC_VECTOR(3 downto 0); -- output of register 7
```

```
constant period : time := 100 ns;
```

```
begin
```

```
UUT : RegBank PORT MAP (
```

```
    RegBank_EN => RegBank_EN,
```

```
    RegBank_Clk => RegBank_Clk,
```

```
    RegBank_Res => RegBank_Res,
```

```
    RegBank_D => RegBank_D,
```

```
    RegBank_Q_0 => RegBank_Q_0,
```

```
    RegBank_Q_1 => RegBank_Q_1,
```

```
    RegBank_Q_2 => RegBank_Q_2,
```

```
    RegBank_Q_3 => RegBank_Q_3,
```

```
    RegBank_Q_4 => RegBank_Q_4,
```

```
    RegBank_Q_5 => RegBank_Q_5,
```

```
    RegBank_Q_6 => RegBank_Q_6,
```

```
    RegBank_Q_7 => RegBank_Q_7  
);
```

```
process  
begin  
    RegBank_Clk <= '0';  
    wait for period/2;  
  
    RegBank_Clk <= '1';  
    wait for period/2 ;  
  
end process;
```

```
--Index 210536 - 11 0011 0110 0110 1000  
--Index 210116 - 11 0011 0100 1100 0100
```

```
process  
begin  
  
    RegBank_EN <= "000"; -- choose Register 0  
    RegBank_Res <= '0';  
    RegBank_D <= "1000";  
  
    wait for period;  
  
    RegBank_EN <= "001"; -- choose Register 1  
    RegBank_Res <= '0';  
    RegBank_D <= "1000";  
  
    wait for period;  
  
    RegBank_EN <= "010"; -- choose Register 2  
    RegBank_Res <= '0';  
    RegBank_D <= "0100";  
  
    wait for period;  
  
    RegBank_EN <= "011"; -- choose Register 3
```

```
RegBank_Res <= '0';  
RegBank_D <= "0011";
```

```
wait for period;
```

```
RegBank_EN <= "100"; -- choose Register 4  
RegBank_Res <= '0';  
RegBank_D <= "1000";
```

```
wait for period;
```

```
RegBank_EN <= "101"; -- choose Register 5  
RegBank_Res <= '0';  
RegBank_D <= "0110";
```

```
wait for period;
```

```
RegBank_EN <= "101"; -- reset register 5  
RegBank_Res <= '1';
```

```
wait for period;
```

```
RegBank_EN <= "110"; -- choose Register 6  
RegBank_Res <= '0';  
RegBank_D <= "1100";
```

```
wait for period;
```

```
RegBank_EN <= "111"; -- choose Register 7  
RegBank_Res <= '0';  
RegBank_D <= "1000";
```

```
wait ;
```

```
end process;
```

```
end Behavioral;
```


Program ROM

Sources

ROM.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

use ieee.numeric_std.all;

entity ROM is
    Port ( address : in STD_LOGIC_VECTOR (2 downto 0);
          data : out STD_LOGIC_VECTOR (11 downto 0));
end ROM;

architecture Behavioral of ROM is
    type rom_type is array (0 to 7) of std_logic_vector(11 downto 0);
    signal program_ROM : rom_type := (

        --main program
        "101110000000", -- MOVI R7,0
        "100010000001", -- MOVI R1,1
        "100100000010", -- MOVI R2,2
        "100110000011", -- MOVI R3,3
        "001110010000", -- ADD R7,R1
        "001110100000", -- ADD R7,R2
        "001110110000", -- ADD R7,R3
        "110000000011" -- JZR R0,6

    );
begin
    data <= program_ROM(to_integer(unsigned(address)));
end Behavioral;
```

Simulations

TB_ROM.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_ROM is
-- Port ( );
end TB_ROM;

architecture Behavioral of TB_ROM is

component ROM
Port ( address : in STD_LOGIC_VECTOR (2 downto 0);
      data : out STD_LOGIC_VECTOR (11 downto 0));
end component;

signal address : STD_LOGIC_VECTOR (2 downto 0);
signal data : STD_LOGIC_VECTOR (11 downto 0);

begin

UUT : ROM PORT MAP (
    address => address,
    data => data
);
process
begin

address <= "000";
wait for 100 ns;

address <= "001";
wait for 100 ns;

address <= "010";
wait for 100 ns;

address <= "011";
```

```
wait for 100 ns;

address <= "100";
wait for 100 ns;

address <= "101";
wait for 100 ns;

address <= "110";
wait for 100 ns;

address <= "111";
wait ;
```

```
end process;
```

```
end Behavioral;
```

Instruction Decoder

Sources

InstructionDecoder.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity InstructionDecoder is
    Port ( InstructionBus : in STD_LOGIC_VECTOR (11 downto 0);
          RegJumpCheck : in STD_LOGIC_VECTOR (3 downto 0);
          RegisterEnable : out STD_LOGIC_VECTOR (2 downto 0);
          LoadSelector : out STD_LOGIC;
          ImmediateValue : out STD_LOGIC_VECTOR (3 downto 0);
          RegisterSelector_A : out STD_LOGIC_VECTOR (2 downto 0);
          RegisterSelector_B : out STD_LOGIC_VECTOR (2 downto 0);
```

```

        AddSubSelector : out STD_LOGIC;
        JumpFlag : out STD_LOGIC;
        JumpAddress : out STD_LOGIC_VECTOR (2 downto 0));
end InstructionDecoder;

```

architecture Behavioral of InstructionDecoder is

```
begin
```

```
process (InstructionBus) begin
```

```
-- MOVI
```

```
if ((InstructionBus(11)='1') AND (InstructionBus(10)='0') ) then
```

```
    RegisterEnable(0) <= InstructionBus(7);
```

```
    RegisterEnable(1) <= InstructionBus(8);
```

```
    RegisterEnable(2) <= InstructionBus(9);
```

```
    LoadSelector <= '0'; -- Choose Immediate Value from MUX
```

```
    ImmediateValue(0) <= InstructionBus(0);
```

```
    ImmediateValue(1) <= InstructionBus(1);
```

```
    ImmediateValue(2) <= InstructionBus(2);
```

```
    ImmediateValue(3) <= InstructionBus(3);
```

```
    JumpFlag <= '0' ; -- not JMP.Just increment address by 1
```

```
end if;
```

```
-- ADD
```

```
if ((InstructionBus(11)='0') AND (InstructionBus(10)='0') ) then
```

```
    RegisterEnable(0) <= InstructionBus(7);
```

```
    RegisterEnable(1) <= InstructionBus(8);
```

```
    RegisterEnable(2) <= InstructionBus(9);
```

```
    RegisterSelector_A(0) <= InstructionBus(7);
```

```
    RegisterSelector_A(1) <= InstructionBus(8);
```

```
    RegisterSelector_A(2) <= InstructionBus(9);
```

```

RegisterSelector_B(0) <= InstructionBus(4);
RegisterSelector_B(1) <= InstructionBus(5);
RegisterSelector_B(2) <= InstructionBus(6);

LoadSelector <= '1'; -- Choose AddSubVal from Mux
AddSubSelector <= '0'; -- select addition
JumpFlag <= '0' ; -- not JMP.Just increment address by 1

```

end if;

-- NEG

```

if ((InstructionBus(11)='0') AND (InstructionBus(10)='1') ) then

```

```

    RegisterEnable(0) <= InstructionBus(7);
    RegisterEnable(1) <= InstructionBus(8);
    RegisterEnable(2) <= InstructionBus(9);

```

```

    LoadSelector <= '1'; --Choose AddSumVal from Mux

```

```

    RegisterSelector_B(0) <= InstructionBus(9);
    RegisterSelector_B(1) <= InstructionBus(8);
    RegisterSelector_B(2) <= InstructionBus(7);

```

```

    RegisterSelector_A(0)<= '0';
    RegisterSelector_A(1)<= '0';
    RegisterSelector_A(2)<= '0';

```

```

    AddSubSelector <= '1';

```

```

    JumpFlag <= '0' ; -- not JMP.Just increment address by 1

```

end if;

-- JZR

```

if ((InstructionBus(11)='1') AND (InstructionBus(10)='1') ) then

```

```

    RegisterEnable(0) <= InstructionBus(7);
    RegisterEnable(1) <= InstructionBus(8);
    RegisterEnable(2) <= InstructionBus(9);

```

```

    RegisterSelector_A(0) <= InstructionBus(7);
    RegisterSelector_A(1) <= InstructionBus(8);

```

```

RegisterSelector_A(2) <= InstructionBus(9);

if (RegJumpCheck = "0000") then

    JumpFlag <= '1' ; -- JMP instruction

    JumpAddress(0) <= InstructionBus(0);
    JumpAddress(1) <= InstructionBus(1);
    JumpAddress(2) <= InstructionBus(2);
else
    JumpFlag <= '0';
end if;

end if;
end process ;

end Behavioral;

```

Simulations

TB_InstructionDecoder.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_InstructionDecoder is
-- Port ( );
end TB_InstructionDecoder;

architecture Behavioral of TB_InstructionDecoder is
component InstructionDecoder
Port ( InstructionBus : in STD_LOGIC_VECTOR (11 downto 0);
      RegJumpCheck : in STD_LOGIC_VECTOR (3 downto 0);
      RegisterEnable : out STD_LOGIC_VECTOR (2 downto 0);
      LoadSelector : out STD_LOGIC;
      ImmediateValue : out STD_LOGIC_VECTOR (3 downto 0);
      RegisterSelector_A : out STD_LOGIC_VECTOR (2 downto 0);
      RegisterSelector_B : out STD_LOGIC_VECTOR (2 downto 0);
      AddSubSelector : out STD_LOGIC;

```

```

        JumpFlag : out STD_LOGIC;
        JumpAddress : out STD_LOGIC_VECTOR (2 downto 0));

end component;

signal InstructionBus : STD_LOGIC_VECTOR (11 downto 0);
signal RegJumpCheck : STD_LOGIC_VECTOR (3 downto 0);
signal RegisterEnable : STD_LOGIC_VECTOR (2 downto 0);
signal LoadSelector : STD_LOGIC;
signal ImmediateValue : STD_LOGIC_VECTOR (3 downto 0);
signal RegisterSelector_A : STD_LOGIC_VECTOR (2 downto 0);
signal RegisterSelector_B : STD_LOGIC_VECTOR (2 downto 0);
signal AddSubSelector : STD_LOGIC;
signal JumpFlag : STD_LOGIC;
signal JumpAddress : STD_LOGIC_VECTOR (2 downto 0);

begin

UUT : InstructionDecoder PORT MAP (
    InstructionBus => InstructionBus,
    RegJumpCheck => RegJumpCheck,
    RegisterEnable => RegisterEnable,
    LoadSelector => LoadSelector,
    ImmediateValue => ImmediateValue,
    RegisterSelector_A => RegisterSelector_A,
    RegisterSelector_B => RegisterSelector_B,
    AddSubSelector=> AddSubSelector,
    JumpFlag => JumpFlag,
    JumpAddress=> JumpAddress

);

process
begin

InstructionBus <= "1000100000001";
wait for 100 ns;

InstructionBus <= "1001000000010";

```

```

wait for 100 ns;

InstructionBus <= "100110000011";
wait for 100 ns;

InstructionBus <= "001110010000";
wait for 100 ns;

InstructionBus <= "001110100000";
wait for 100 ns;

InstructionBus <= "001110110000";
wait for 100 ns;

InstructionBus <= "110000000110";
RegJumpCheck <= "0000"; -- set manually to zero to execute JMP
wait for 100 ns;

InstructionBus <= "110000000110";
RegJumpCheck <= "0001"; -- set manually to non zero to not JMP
wait for 100 ns;

InstructionBus <= "000000000000";
wait;

end process ;

```

System (slow clock+nano processor+7 segment ROM)

Sources

nano_processor.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity nano_processor is
    Port ( Clk : in STD_LOGIC;

```



```

    Res : in STD_LOGIC;
    Overflow : out STD_LOGIC;
    Zero : out STD_LOGIC;
    Output : out STD_LOGIC_VECTOR (3 downto 0));
end nano_processor;

```

architecture Behavioral of nano_processor is

```

component Mux_2_to_1_bit_3
Port ( S : in STD_LOGIC;
      D0 : in STD_LOGIC_VECTOR (2 downto 0);
      D1 : in STD_LOGIC_VECTOR (2 downto 0);
      Y : out STD_LOGIC_VECTOR (2 downto 0));

```

```

end component;

```

```

component Mux_2_to_1_bit_4
Port ( S : in STD_LOGIC;
      D0 : in STD_LOGIC_VECTOR (3 downto 0);
      D1 : in STD_LOGIC_VECTOR (3 downto 0);
      Y : out STD_LOGIC_VECTOR (3 downto 0));
end component;

```

```

component Adder_3bit
Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
      S : out STD_LOGIC_VECTOR (2 downto 0));
end component;

```

```

component Mux_8_to_1_bit_4
Port ( S : in STD_LOGIC_VECTOR (2 downto 0);
      D0 : in STD_LOGIC_VECTOR (3 downto 0);
      D1 : in STD_LOGIC_VECTOR (3 downto 0);
      D2 : in STD_LOGIC_VECTOR (3 downto 0);
      D3 : in STD_LOGIC_VECTOR (3 downto 0);
      D4 : in STD_LOGIC_VECTOR (3 downto 0);
      D5 : in STD_LOGIC_VECTOR (3 downto 0);
      D6 : in STD_LOGIC_VECTOR (3 downto 0);
      D7 : in STD_LOGIC_VECTOR (3 downto 0);
      Y : out STD_LOGIC_VECTOR (3 downto 0));
end component;

```

component ASUnit

```
Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
      B : in STD_LOGIC_VECTOR (3 downto 0);
      Selector : in STD_LOGIC;
      S : out STD_LOGIC_VECTOR (3 downto 0);
      Zero : out STD_LOGIC;
      Overflow : out STD_LOGIC);
end component;
```

component InstructionDecoder

```
Port ( InstructionBus : in STD_LOGIC_VECTOR (11 downto 0);
      RegJumpCheck : in STD_LOGIC_VECTOR (3 downto 0);
      RegisterEnable : out STD_LOGIC_VECTOR (2 downto 0);
      LoadSelector : out STD_LOGIC;
      ImmediateValue : out STD_LOGIC_VECTOR (3 downto 0);
      RegisterSelector_A : out STD_LOGIC_VECTOR (2 downto 0);
      RegisterSelector_B : out STD_LOGIC_VECTOR (2 downto 0);
      AddSubSelector : out STD_LOGIC;
      JumpFlag : out STD_LOGIC;
      JumpAddress : out STD_LOGIC_VECTOR (2 downto 0));
end component;
```

component ProgramCounter

```
Port ( D : in STD_LOGIC_VECTOR (2 downto 0);
      Res : in STD_LOGIC;
      Clk : in STD_LOGIC;
      Q : out STD_LOGIC_VECTOR (2 downto 0));
end component;
```

component ROM

```
Port ( address : in STD_LOGIC_VECTOR (2 downto 0);
      data : out STD_LOGIC_VECTOR (11 downto 0));
end component;
```

component RegBank

```
Port (
  RegBank_EN : in STD_LOGIC_VECTOR(2 downto 0); -- Register enable which selects the
  register
  RegBank_Clk : in STD_LOGIC;
```

```

RegBank_Res : in STD_LOGIC ;
RegBank_D : in STD_LOGIC_VECTOR(3 downto 0); -- input of register bank

-- output of register bank
RegBank_Q_0 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 0
RegBank_Q_1 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 1
RegBank_Q_2 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 2
RegBank_Q_3 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 3
RegBank_Q_4 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 4
RegBank_Q_5 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 5
RegBank_Q_6 : out STD_LOGIC_VECTOR(3 downto 0); -- output of register 6
RegBank_Q_7 : out STD_LOGIC_VECTOR(3 downto 0) -- output of register 7
);
end component;

signal Out_Mux_2_to_1_bit_3 : STD_LOGIC_VECTOR(2 downto 0) := "000";

signal MemorySelect : STD_LOGIC_VECTOR(2 downto 0) := "000";

signal Out_Adder_3bit : STD_LOGIC_VECTOR(2 downto 0) := "000";

signal JumpFlag : STD_LOGIC := '0';
signal JumpAddress : STD_LOGIC_VECTOR(2 downto 0) := "000";
signal InstructionBus : STD_LOGIC_VECTOR(11 downto 0) := "0000000000000";
signal RegisterEnable : STD_LOGIC_VECTOR(2 downto 0) := "000";
signal LoadSelector : STD_LOGIC := '0';
signal ImmediateValue : STD_LOGIC_VECTOR(3 downto 0) := "0000" ;
signal RegisterSelector_A : STD_LOGIC_VECTOR(2 downto 0) := "000" ;
signal RegisterSelector_B : STD_LOGIC_VECTOR(2 downto 0) := "000";
signal AddSubSelector : STD_LOGIC := '0' ;
signal RegJumpCheck : STD_LOGIC_VECTOR(3 downto 0) := "0000" ;

signal RegBank_Q_0 : STD_LOGIC_VECTOR(3 downto 0) := "0000"; -- output of register 0
signal RegBank_Q_1 : STD_LOGIC_VECTOR(3 downto 0) := "0000"; -- output of register 1
signal RegBank_Q_2 : STD_LOGIC_VECTOR(3 downto 0) := "0000"; -- output of register 2
signal RegBank_Q_3 : STD_LOGIC_VECTOR(3 downto 0) := "0000"; -- output of register 3
signal RegBank_Q_4 : STD_LOGIC_VECTOR(3 downto 0) := "0000"; -- output of register 4
signal RegBank_Q_5 : STD_LOGIC_VECTOR(3 downto 0) := "0000"; -- output of register 5
signal RegBank_Q_6 : STD_LOGIC_VECTOR(3 downto 0) := "0000"; -- output of register 6
signal RegBank_Q_7 : STD_LOGIC_VECTOR(3 downto 0) := "0000"; -- output of register 7

```

```
signal Out_Mux_B : STD_LOGIC_VECTOR(3 downto 0):= "0000";
```

```
signal RegBank_D : STD_LOGIC_VECTOR(3 downto 0) := "0000";
```

```
signal Out_ASUnit : STD_LOGIC_VECTOR(3 downto 0) := "0000";
```

```
begin
```

```
-- 2-way 3-bit Mux
```

```
Mux_2_to_1_bit_3_0 : Mux_2_to_1_bit_3
```

```
port map (
```

```
    S => JumpFlag,
```

```
    D0=> Out_Adder_3bit, -- JumpFlag = 0
```

```
    D1=> JumpAddress, -- JumpFlag = 1
```

```
    Y => Out_Mux_2_to_1_bit_3
```

```
);
```

```
Adder_3bit_0 : Adder_3bit
```

```
port map(
```

```
    A => MemorySelect,
```

```
    S => Out_Adder_3bit
```

```
);
```

```
ProgramCounter_0 : ProgramCounter
```

```
port map(
```

```
    D => Out_Mux_2_to_1_bit_3,
```

```
    Res => Res,
```

```
    Clk => Clk,
```

```
    Q => MemorySelect
```

```
);
```

```
ROM_0 : ROM
```

```
port map(
```

```
    address => MemorySelect,
```

```
    data => InstructionBus
```

```
);
```

InstructionDecoder_0 : InstructionDecoder

port map(

InstructionBus => InstructionBus,
RegJumpCheck => RegJumpCheck,
RegisterEnable => RegisterEnable,
LoadSelector => LoadSelector,
ImmediateValue => ImmediateValue,
RegisterSelector_A => RegisterSelector_A,
RegisterSelector_B => RegisterSelector_B,
AddSubSelector => AddSubSelector,
JumpFlag => JumpFlag,
JumpAddress => JumpAddress

);

RegBank_0 : RegBank

port map(

RegBank_EN => RegisterEnable, -- Register enable which selects the register
RegBank_Clk => Clk,
RegBank_Res => Res,
RegBank_D => RegBank_D , -- input of register bank

-- output of register bank

RegBank_Q_0 => RegBank_Q_0, -- output of register 0
RegBank_Q_1 => RegBank_Q_1, -- output of register 1
RegBank_Q_2 => RegBank_Q_2, -- output of register 2
RegBank_Q_3 => RegBank_Q_3, -- output of register 3
RegBank_Q_4 => RegBank_Q_4, -- output of register 4
RegBank_Q_5 => RegBank_Q_5, -- output of register 5
RegBank_Q_6 => RegBank_Q_6, -- output of register 6
RegBank_Q_7 => RegBank_Q_7 -- output of register 7

);

Mux_8_to_1_bit_4_A : Mux_8_to_1_bit_4

port map(

S => RegisterSelector_A,

```

D0=> RegBank_Q_0,
D1=> RegBank_Q_1,
D2=> RegBank_Q_2,
D3=> RegBank_Q_3,
D4=> RegBank_Q_4,
D5=> RegBank_Q_5,
D6=> RegBank_Q_6,
D7=> RegBank_Q_7,
Y => RegJumpCheck
);

```

```

Mux_8_to_1_bit_4_B : Mux_8_to_1_bit_4
port map(
    S => RegisterSelector_B,
    D0=> RegBank_Q_0,
    D1=> RegBank_Q_1,
    D2=> RegBank_Q_2,
    D3=> RegBank_Q_3,
    D4=> RegBank_Q_4,
    D5=> RegBank_Q_5,
    D6=> RegBank_Q_6,
    D7=> RegBank_Q_7,
    Y => Out_Mux_B
);

```

```

ASUnit_0 : ASUnit
port map (
    A => RegJumpCheck,
    B => Out_Mux_B,
    Selector => AddSubSelector,
    S => Out_ASUnit,
    Zero => Zero,
    Overflow => Overflow
);

```

```

Mux_2_to_1_bit_4_0 : Mux_2_to_1_bit_4
port map(
    S => LoadSelector,
    D0 => ImmediateValue,

```

```

    D1 => Out_ASUnit,
    Y => RegBank_D
);

Output <= RegBank_Q_7;

end Behavioral;

```

System.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity System is
    Port (
        Clk : in STD_LOGIC;
        Res : in STD_LOGIC;
        Zero: out STD_LOGIC;
        Overflow: out STD_LOGIC;
        S_7Seg : out STD_LOGIC_VECTOR(6 downto 0);
        S_out : out STD_LOGIC_VECTOR(3 downto 0);
        Anode : out STD_LOGIC_VECTOR(3 downto 0)
    );
end System;

architecture Behavioral of System is

    component nano_processor
        Port ( Clk : in STD_LOGIC;
              Res : in STD_LOGIC;
              Overflow : out STD_LOGIC;
              Zero : out STD_LOGIC;
              Output : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    component LUT_16_7
        Port ( address : in STD_LOGIC_VECTOR (3 downto 0);

```

```

        data : out STD_LOGIC_VECTOR (6 downto 0));
end component;

component Slow_Clk
Port ( Clk_in : in STD_LOGIC;
      Clk_out : out STD_LOGIC);
end component;

signal Slow_Clk_out : STD_LOGIC;
signal Reg7out : STD_LOGIC_VECTOR(3 downto 0);

begin

Slow_Clk_0 : Slow_Clk
port map(
Clk_in => Clk,
Clk_out => Slow_Clk_out
);

nano_processor_0 : nano_processor
port map(
Clk => Slow_Clk_out,
Res => Res,
Overflow => Overflow,
Zero => Zero,
Output => Reg7out
);

LUT_16_7_0 : LUT_16_7
port map(
address => Reg7out,
data => S_7Seg
);

S_out <= Reg7out;
Anode <= "1110";
end Behavioral;

```

Slow_Clk.vhd


```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Slow_Clk is
  Port ( Clk_in : in STD_LOGIC;
        Clk_out : out STD_LOGIC);
end Slow_Clk;

architecture Behavioral of Slow_Clk is

  signal count:integer:=1;
  signal clk_status:std_logic:='0';

begin
  process(Clk_in) begin

    if(rising_edge(Clk_in)) then
      count<=count+1;
      if(count=30000000) then
        clk_status<= not clk_status;
        Clk_out<=clk_status;
        count<=1;
      end if;
    end if;

  end process;

```

7 segment ROM

LUT_16_7.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

use ieee.numeric_std.all;

entity LUT_16_7 is
  Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
        data : out STD_LOGIC_VECTOR (6 downto 0));

```

```
end LUT_16_7;
```

architecture Behavioral of LUT_16_7 is

```
type rom_type is array (0 to 15) of std_logic_vector(6 downto 0);
```

```
    signal sevenSegment_ROM : rom_type := (
```

```
        "1000000", -- 0
```

```
        "1111001", -- 1
```

```
        "0100100", -- 2
```

```
        "0110000", -- 3
```

```
        "0011001", -- 4
```

```
        "0010010", -- 5
```

```
        "0000010", -- 6
```

```
        "1111000", -- 7
```

```
        "0000000", -- 8
```

```
        "0010000", -- 9
```

```
        "0001000", -- a
```

```
        "0000011", -- b
```

```
        "1000110", -- c
```

```
        "0100001", -- d
```

```
        "0000110", -- e
```

```
        "0001110" -- f
```

```
    );
```

```
begin
```

```
    data <= sevenSegment_ROM(to_integer(unsigned(address)));
```

```
end Behavioral;
```

Simulations

TB_Slow_Clk.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity TB_Slow_Clk is
```

```
-- Port ( );
```

```
end TB_Slow_Clk;
```

architecture Behavioral of TB_Slow_Clk is

```
component Slow_Clk
```

```
Port ( Clk_in : in STD_LOGIC;  
      Clk_out : out STD_LOGIC);  
end component;
```

```
signal Clk_in : STD_LOGIC;  
signal Clk_out : STD_LOGIC;
```

```
constant period : time := 10 ns;
```

```
begin  
UUT : Slow_Clk PORT MAP(  
    Clk_in => Clk_in,  
    Clk_out => Clk_out  
);
```

```
process  
begin  
  
    Clk_in <= '0';  
    wait for period/2;
```

```
    Clk_in <= '1';  
    wait for period/2;
```

```
end process;
```

```
end Behavioral;
```

TB_nano_processor.vhd

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity TB_nano_processor is  
-- Port ( );  
end TB_nano_processor;
```

```
architecture Behavioral of TB_nano_processor is
```

```
component nano_processor
Port ( Clk : in STD_LOGIC;
      Res : in STD_LOGIC;
      Overflow : out STD_LOGIC;
      Zero : out STD_LOGIC;
      Output : out STD_LOGIC_VECTOR (3 downto 0));
end component;
```

```
signal Clk : STD_LOGIC;
signal Res : STD_LOGIC;
signal Overflow : STD_LOGIC;
signal Zero : STD_LOGIC;
signal Output : STD_LOGIC_VECTOR (3 downto 0);
```

```
constant period : time := 100 ns;
```

```
begin
  UUT : nano_processor PORT MAP (
    Clk => Clk,
    Res => Res,
    Overflow => Overflow,);
```

```
process
begin
  Clk <= '0';
  wait for period/2;
```

```
  Clk <= '1';
  wait for period/2;
end process;
```

```
process
begin
  Res <= '1';
  wait for period;
```

```
  Res <= '0';
  wait;
end process;
```

```
end Behavioral;
```

TB_System.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity TB_System is
```

```
-- Port ( );
```

```
end TB_System;
```

```
architecture Behavioral of TB_System is
```

```
component System
```

```
    Port (
```

```
    Clk : in STD_LOGIC;
```

```
    Res : in STD_LOGIC;
```

```
    Zero: out STD_LOGIC;
```

```
    Overflow: out STD_LOGIC;
```

```
    S_7Seg : out STD_LOGIC_VECTOR(6 downto 0);
```

```
    S_out : out STD_LOGIC_VECTOR(3 downto 0)
```

```
    );
```

```
end component;
```

```
signal Clk : STD_LOGIC;
```

```
signal Res : STD_LOGIC;
```

```
signal Zero: STD_LOGIC;
```

```
signal Overflow: STD_LOGIC;
```

```
signal S_7Seg : STD_LOGIC_VECTOR(6 downto 0);
```

```
signal S_out : STD_LOGIC_VECTOR(3 downto 0);
```

```
constant period : time := 10 ns;
```

```
begin
```

```
UUT : System PORT MAP(
```

```
    Clk => Clk,
```

```
    Res => Res,
```

```
Zero => Zero,  
Overflow => Overflow,  
S_7Seg => S_7Seg,  
S_out => S_out  
);
```

```
process  
begin  
Clk <= '0';  
wait for period/2;
```

```
Clk <= '1';  
wait for period/2;  
end process;
```

```
process  
begin  
Res <= '1';  
wait for period;
```

```
Res <= '0';  
wait;  
end process;
```

```
end Behavioral;
```

Constraint File

```
## Clock signal
set_property PACKAGE_PIN W5 [get_ports Clk]
    set_property IOSTANDARD LVCMOS33 [get_ports Clk]
    create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports Clk]
## LEDs
set_property PACKAGE_PIN U16 [get_ports {S_out[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_out[0]}]
set_property PACKAGE_PIN E19 [get_ports {S_out[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_out[1]}]
set_property PACKAGE_PIN U19 [get_ports {S_out[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_out[2]}]
set_property PACKAGE_PIN V19 [get_ports {S_out[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_out[3]}]
set_property PACKAGE_PIN P1 [get_ports {Zero}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Zero}]
set_property PACKAGE_PIN L1 [get_ports {Overflow}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Overflow}]
##7 segment display
set_property PACKAGE_PIN W7 [get_ports {S_7Seg[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[0]}]
set_property PACKAGE_PIN W6 [get_ports {S_7Seg[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[1]}]
set_property PACKAGE_PIN U8 [get_ports {S_7Seg[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[2]}]
set_property PACKAGE_PIN V8 [get_ports {S_7Seg[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[3]}]
set_property PACKAGE_PIN U5 [get_ports {S_7Seg[4]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[4]}]
set_property PACKAGE_PIN V5 [get_ports {S_7Seg[5]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[5]}]
set_property PACKAGE_PIN U7 [get_ports {S_7Seg[6]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {S_7Seg[6]}]
set_property PACKAGE_PIN U2 [get_ports {Anode[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Anode[0]}]
set_property PACKAGE_PIN U4 [get_ports {Anode[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Anode[1]}]
set_property PACKAGE_PIN V4 [get_ports {Anode[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {Anode[2]}]
```


```
set_property PACKAGE_PIN W4 [get_ports {Anode[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Anode[3]}]
```

##Buttons


```
set_property PACKAGE_PIN U18 [get_ports {Res}]
set_property IOSTANDARD LVCMOS33 [get_ports {Res}]
```

4) All Timing Diagrams


1) ASUnit

 


2) 3-bit adder

 


3) 2-way 3-bit MUX

 


4) 2-way 4-bit MUX

 

5) 8-way 4-bit MUX

 


7) ROM

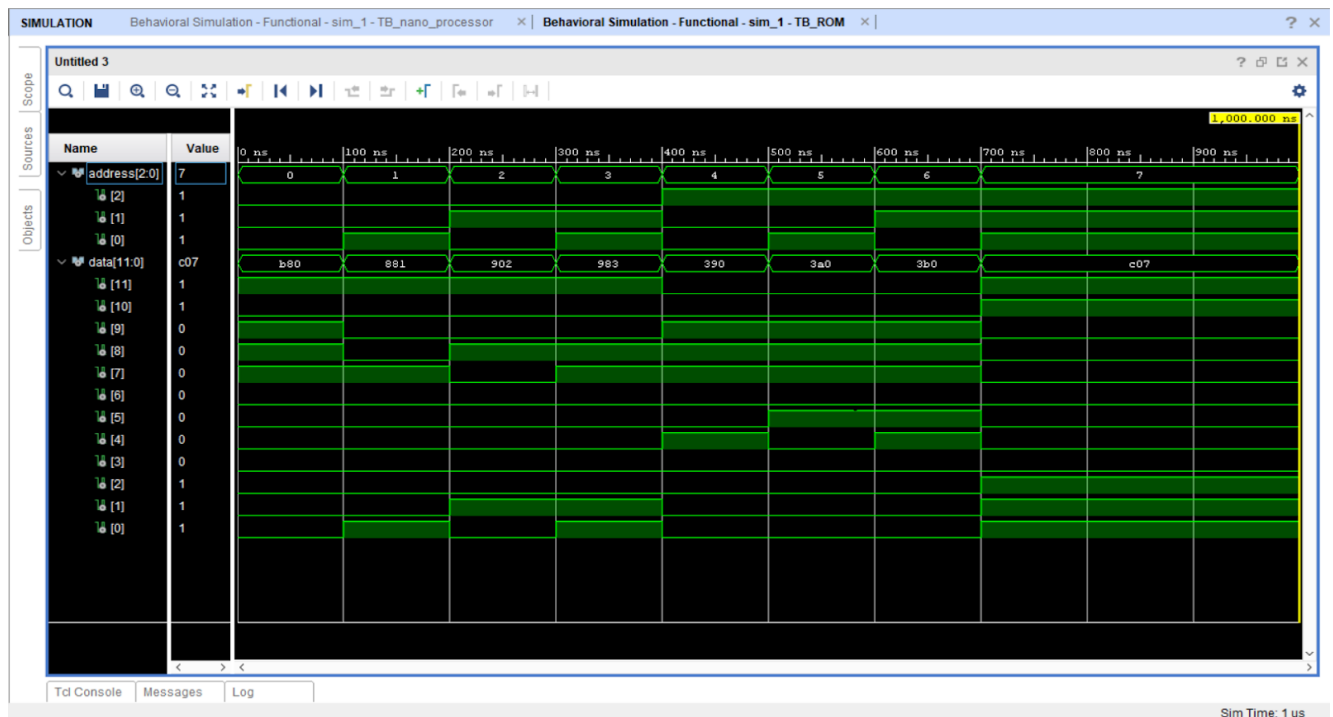


8) Instruction Decoder

Part-1

 


Part-2

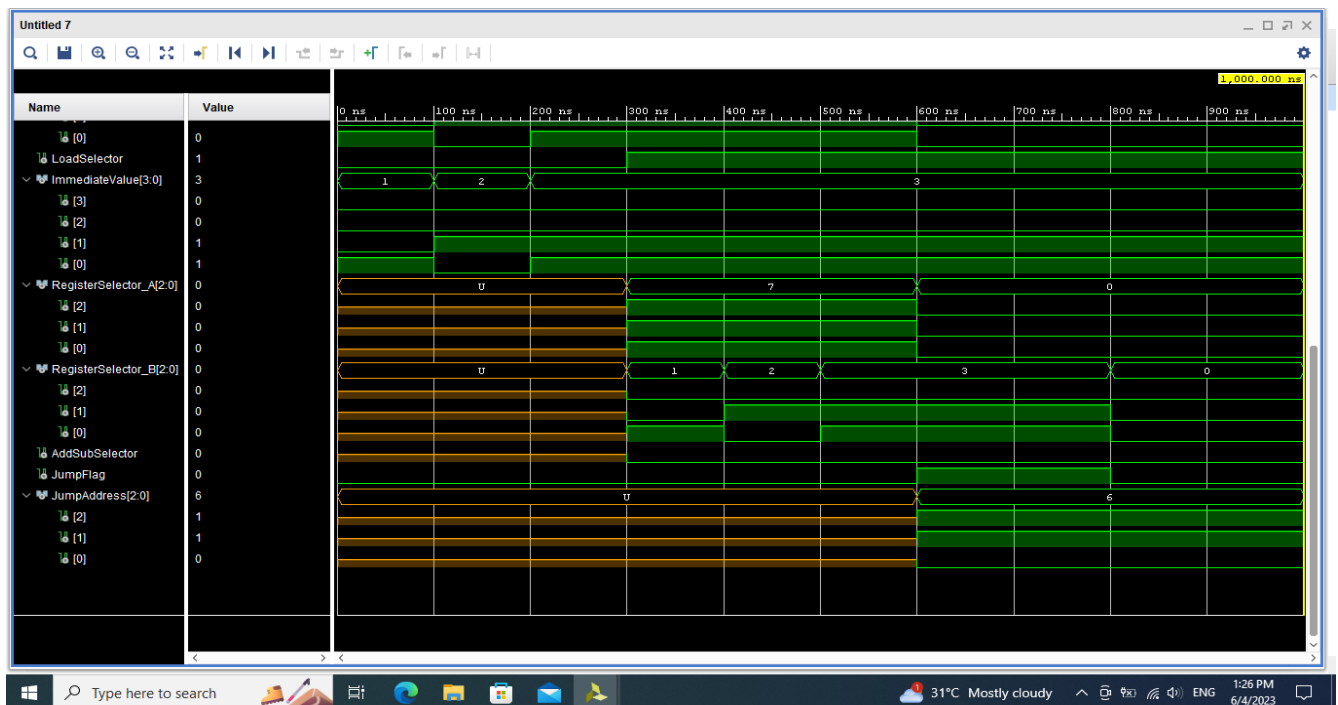


9) Register Bank


Part-1

 


Part-2

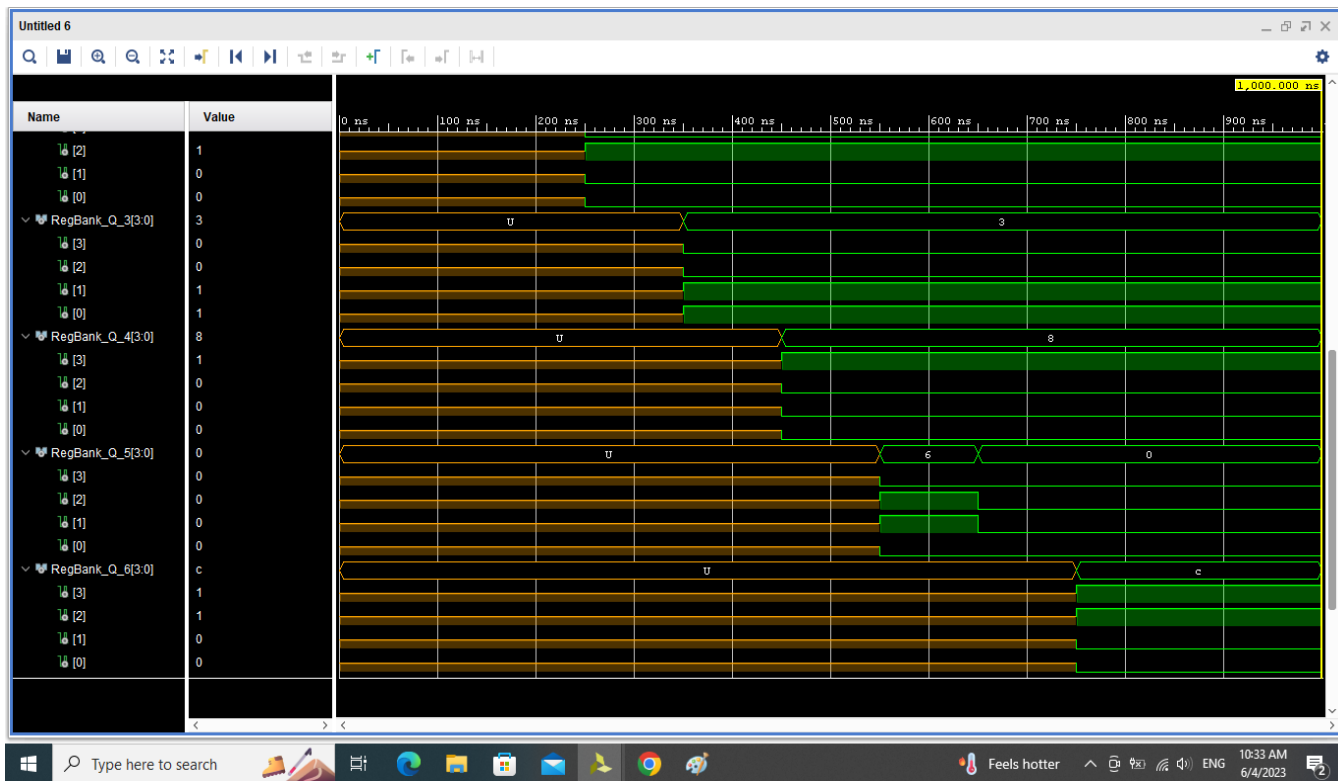


Part-3

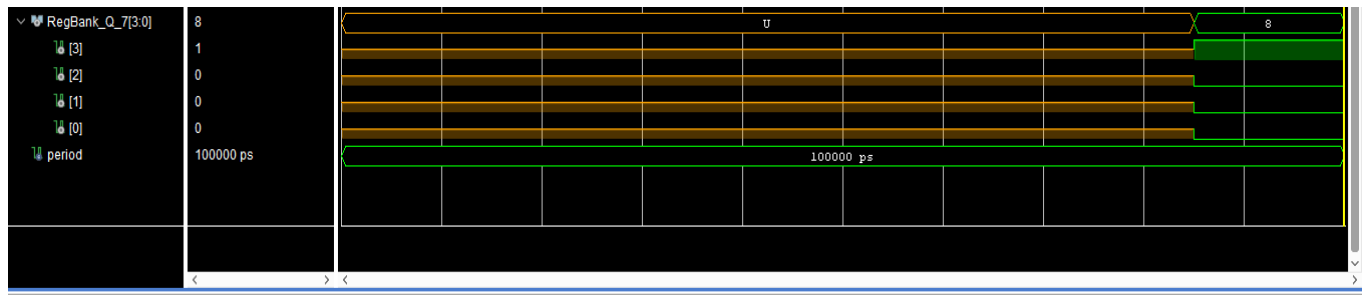

10) Slow Clock

 

11) Nano Processor

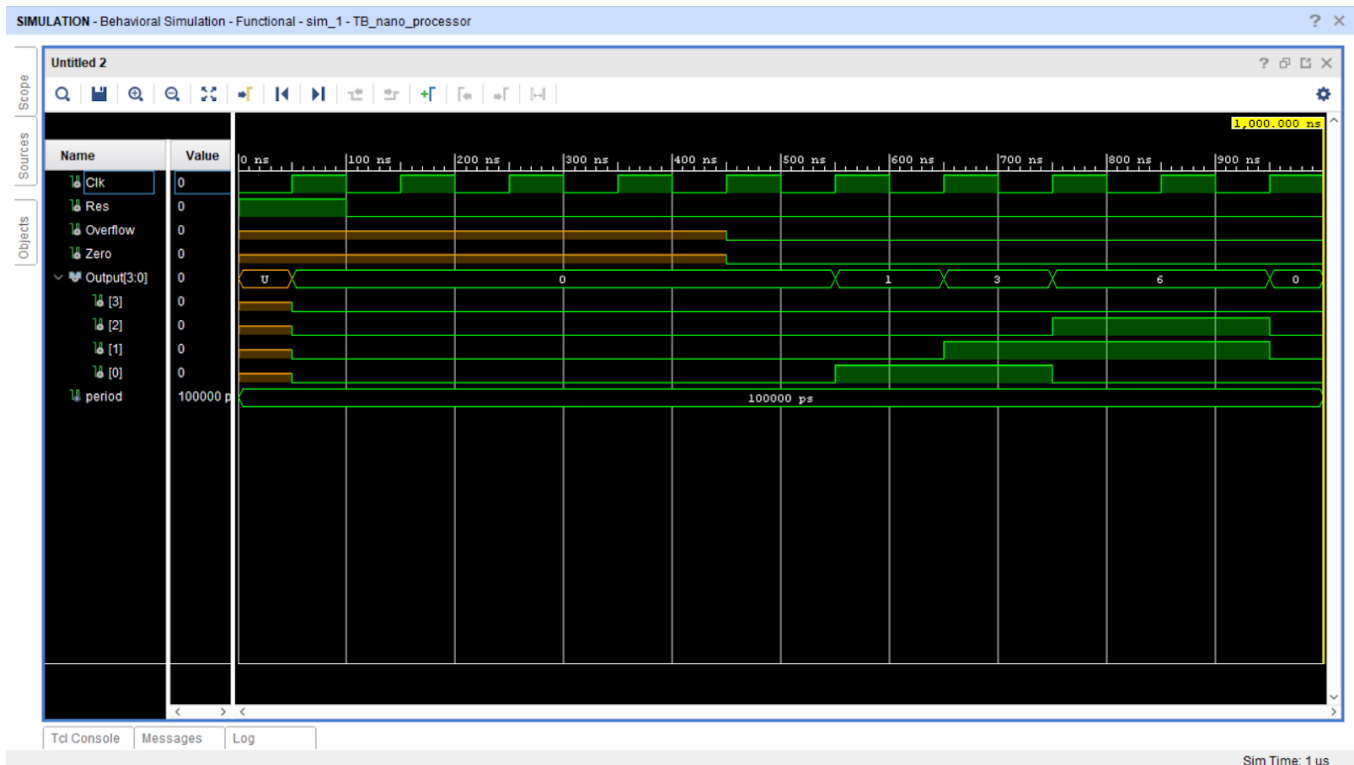

Conclusion

- In this lab we were able to verify the accuracy of our design by simulating and testing every component.
- Instead of using many parallel wires we used buses to design the circuit.
- This simple nano processor design could be extended to build a complex processor which could be able to do complex operations.
- Even though this processor satisfied our work we cannot work on larger problems since the processor is 4-bit wide.
- In this exercise we had to hard code assembly instructions as binary values because the microprocessor only understands machine language.
- Finally this project helped us to build our team work ability and instructors guided us to achieve this task.
- We add a program to calculate $1+2+3$ in to the ROM. We tested our processor in other different programs to check whether other instructions such as NEG are working well.

Contribution by each member

W.T Rathnayaka: 210536K - 30 hours

Wrote source code for each component. Wrote constraint file. Assembling different components to make **nano_processor.vhd**

Dewpura L.C.I.K: 210116A - 20 hours

Wrote source code for **System.vhd** assembling slow clock, 7 seven segment ROM and nano processor. Wrote test bench files for each component.

GitHub Link for all source codes

<https://github.com/Ishdew/Nano-Processor>